



SINUSOIDAL STEADY-STATE ANALYSIS

FINDING THE PARTICULAR SOL<sup>n</sup> WHEN THE FORCING FUNCTION IS SINUSOIDAL

I THE IMPORTANCE OF SINUSOIDS:

- ARISE IN THE NATURAL SOL<sup>s</sup> OF RESONANT CIRCUITS (SYSTEMS)
- ELECTRICAL POWER IS DISTRIBUTED VIA SINUSOIDAL VOLTAGES
- SINUSOIDS OF DIFFERENT FREQ. ARE ORTHOGONAL

LET  $x_1(t) = \cos(\omega_1 t + \phi_1)$  ,  $x_2(t) = \cos(\omega_2 t + \phi_2)$

THEN


$\lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T}^T x_1(t) x_2(t) dt = 0$  IF  $\omega_1 \neq \omega_2$

(THERE ARE A NUMBER OF WAVEFORMS WITH THIS SPECIAL PROPERTY)

- BECAUSE OF ORTHOGONALITY, ANY PERIODIC WAVEFORM CAN BE CREATED AS A SUMMATION OF SINUSOIDS. (FOURIER ANALYSIS)

SINUSOIDS ARE BASIC

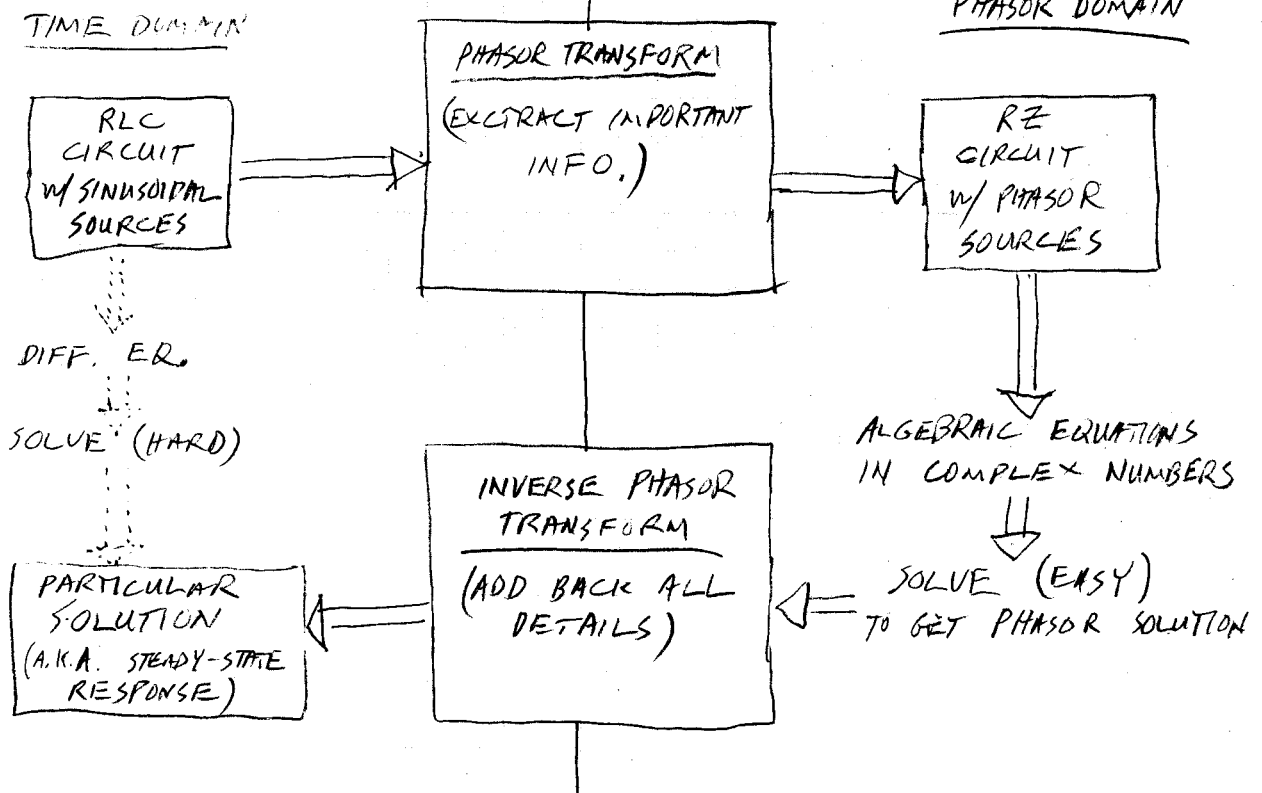II A BIRD'S-EYE VIEW OF SINUSOIDAL ANALYSIS



TRANSFORM — A CHANGE IN MATHEMATICAL DESCRIPTION (USUALLY DONE TO FACILITATE SOLUTION OR TO GAIN INSIGHT FROM A NEW PERSPECTIVE)



III TRANSFORMING SINUSOIDS TO PHASORS

SUPPOSE  $v(t) = V_m \cos(\omega t + \theta)$   $\omega$  IN RAD/SEC.  $\theta$  IN RAD

OR  $v(t) = V_m \cos(2\pi f t + \frac{2\pi \phi}{360})$   $f$  IN HZ  $\phi$  IN DEGREES

A NOTE ON NOTATION: THE NOTATION  $v(t) = V_m \cos(2\pi 60t + 30^\circ)$  IS COMMON. IT SHOULD BE UNDERSTOOD AS

$$v(t) = V_m \cos(120\pi t + \frac{2\pi \cdot 30}{360})$$

THE NOTATION OF "30°" FOR  $\frac{2\pi \cdot 30}{360}$  IS A COMMON SHORT-HAND (SLANG)

- USUALLY  $\omega$  OR  $f$  IS KNOWN FROM CONTEXT

e.g. KDCR IS 88.5 MHz ( $f$ )


e.g. AC POWER IN THE U.S. IS 60 HZ ( $f$ )

- AND THE FORCED RESPONSE ALWAYS HAS THE SAME FREQ. AS THE FORCING FUNCTION

- THEREFORE NO NEED TO SOLVE FOR  $f$  OR  $\omega$

- THE ONLY INTERESTING NUMBERS NEEDED FOR THE SOLUTION ARE AMPLITUDE AND PHASE

- CONSIDER THEM TO FORM A COMPLEX NUMBER

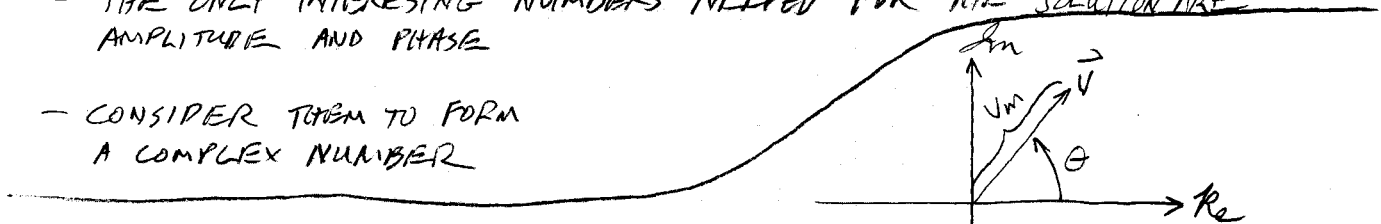

IF  $v(t) = V_m \cos(\omega t + \theta)$

WE CAN WRITE  $\vec{V} = V_m / \theta$  AND UNDERSTAND WHAT IT MEANS.

THIS IS THE PHASOR TRANSFORM OF A SIGNAL

TIME DOMAIN

PHASOR DOMAIN


$i(t) = I_m \cos(\omega t + \theta)$

$\vec{I} = I_m / \theta$

NOTE:  $i(t)$  IS A FUNCTION (OF TIME)

NOTE  $\vec{I}$  IS A COMPLEX NUMBER

INTERLUDE - REVIEW COMPLEX NUMBERS

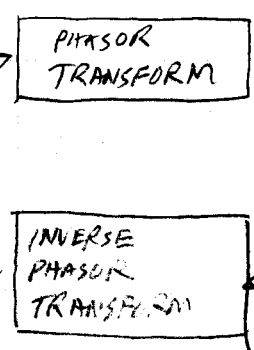



IV APPLICATION OF EULER'S RULE TO PHASORS

$$\begin{aligned}
 v(t) &= V_m \cos(\omega t + \theta) \\
 &= V_m \operatorname{Re} \{ \cos \omega t + \theta + j \sin \omega t + \theta \} \\
 &= V_m \operatorname{Re} \{ e^{j(\omega t + \theta)} \} \\
 &= V_m \operatorname{Re} \{ e^{j\theta} \} \operatorname{Re} \{ e^{j\omega t} \}
 \end{aligned}$$

TAKE PHASOR TRANSFORM (DIVIDE THRU BY  $\operatorname{Re} \{ e^{j\omega t} \}$ ) AND JOIN  $\{ e^{j\theta} \}$

$$\bar{V} = V_m e^{j\theta}$$



↑  
SCALING

↑  
ADDITIVITY

$$\bar{V} = V_m \angle \theta$$


∴ BY SUPERPOSITION, WE OUGHT TO BE ABLE TO SOLVE CCT PROBLEMS USING PHASORS RATHER THAN FUNCTIONS

eg FIND  $i'$

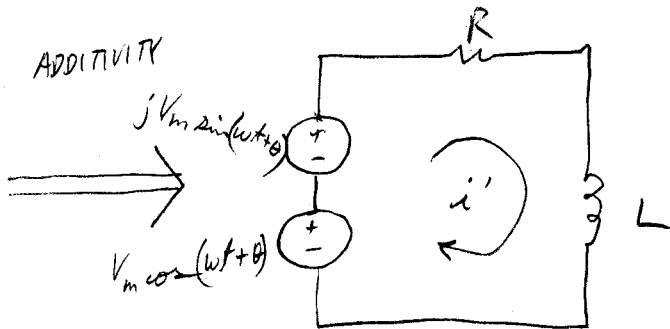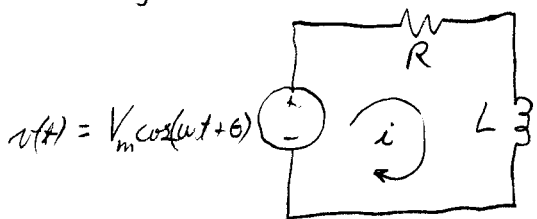

→ ASSUME  $i'(t) = I_m e^{j(\omega t + \phi)}$
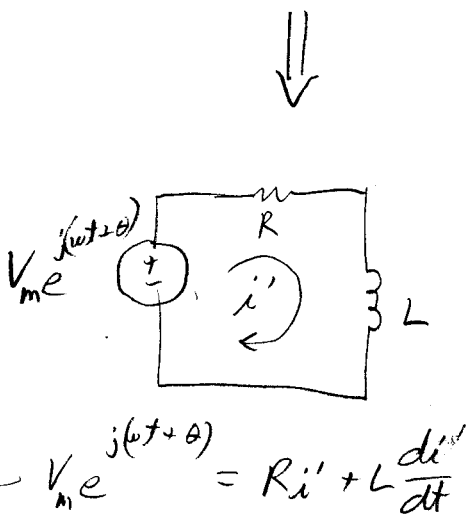
$$\begin{aligned}
 \frac{di'}{dt} &= j\omega I_m e^{j(\omega t + \phi)} \\
 V_m e^{j(\omega t + \theta)} &= R I_m e^{j(\omega t + \phi)} + L j\omega I_m e^{j(\omega t + \phi)} \\
 V_m e^{j\theta} &= R I_m e^{j\phi} + j\omega L I_m e^{j\phi} \\
 V_m e^{j\theta} &= (R + j\omega L) I_m e^{j\phi} \\
 I_m e^{j\phi} &= \frac{V_m e^{j\theta}}{(R + j\omega L)}
 \end{aligned}$$



THE PROCESS IS JUST LIKE DC ANALYSIS! (ONLY USING COMPLEX NUMBERS)



V APPLICATION OF PHASOR CONCEPT TO SIMPLE CIRCUIT ELEMENTS

A.) FOR AN INDUCTOR

TIME DOMAIN

PHASOR DOMAIN

$$\text{LET } i = I_m \cos(\omega t + \theta) \longrightarrow \text{LET } \bar{I} = I_m \angle \theta \quad (= I_m e^{j\theta})$$

$$\downarrow$$

$$v = L \frac{di}{dt}$$

$$v = -I_m \omega L \sin(\omega t + \theta)$$

$$v = I_m \omega L \cos(\omega t + \theta + 90^\circ)$$

$$\longrightarrow \bar{V} = I_m \omega L \angle \theta + 90^\circ$$

$$\bar{V} = (I_m \angle \theta) (\omega L \angle 90^\circ)$$

$$\bar{V} = (I_m \angle \theta) (j\omega L)$$

$$\therefore \frac{\bar{V}}{\bar{I}} = j\omega L \text{ FOR AN INDUCTOR}$$

B.) FOR A CAPACITOR

$$\text{LET } v = V_m \cos(\omega t + \theta) \longrightarrow \bar{V} = V_m \angle \theta \quad (= V_m e^{j\theta})$$

$$\downarrow$$

$$i = C \frac{dv}{dt}$$

$$i = -V_m \omega C \sin(\omega t + \theta)$$

$$i = V_m \omega C \cos(\omega t + \theta + 90^\circ)$$

$$\longrightarrow \bar{I} = V_m \omega C \angle \theta + 90^\circ$$

$$\bar{I} = (V_m \angle \theta) (\omega C \angle 90^\circ)$$

$$\bar{I} = (V_m \angle \theta) (j\omega C)$$

$$\therefore \frac{\bar{V}}{\bar{I}} = \frac{1}{j\omega C} \text{ FOR A CAPACITOR}$$

C.) FOR A RESISTOR

$$\text{LET } i = I_m \cos(\omega t + \theta) \longrightarrow \bar{I} = I_m \angle \theta$$

$$v = R I_m \cos(\omega t + \theta)$$

$$\bar{V} = R I_m \angle \theta$$

$$\therefore \frac{\bar{V}}{\bar{I}} = R$$



D) DEFINITION OF IMPEDANCE (AND ADMITTANCE)

RESISTANCE IS THE RATIO  $R = \frac{V}{I}$ .

IF WE GENERALIZE THIS TO PHASORS, WE HAVE IMPEDANCE.

defn IMPEDANCE IS THE RATIO OF PHASORS  $\bar{Z} = \frac{\bar{V}}{\bar{I}}$

ALTHOUGH  $\bar{Z}$  IS A COMPLEX NUMBER IT IS NOT A PHASOR BECAUSE IT DOES NOT REPRESENT A SINUSOID.

THE IMPEDANCE OF SIMPLE CIRCUIT ELEMENTS IS:

RESISTOR:	$\bar{Z} = R$
INDUCTOR	$\bar{Z} = j\omega L$
CAPACITOR	$\bar{Z} = \frac{1}{j\omega C}$

NOTE THAT IN GENERAL, IMPEDANCE IS A FUNCTION OF FREQUENCY ( $\omega$ )

IMPEDANCE HAS UNITS OF OHMS

JUST AS THE RECIPROCAL OF RESISTANCE IS CONDUCTANCE (IN SIEMENS)

THE RECIPROCAL OF IMPEDANCE IS ADMITTANCE (ALSO IN SIEMENS)

defn  $G = \frac{1}{R} \rightarrow \bar{Y} = \frac{1}{\bar{Z}} = \frac{\bar{I}}{\bar{V}}$

E) OBSERVATIONS ABOUT IMPEDANCE (AND ADMITTANCE)

- IMPEDANCE IS A COMPLEX NUMBER. IT IS NOT A PHASOR BECAUSE IT CAN'T BE TRANSFORMED BACK TO THE TIME DOMAIN IT DOES NOT REPRESENT A SINUSOID.

- IMPEDANCE IS A COMPLEX NUMBER, IT HAS A REAL AND AN IMAGINARY PART

observation:  $\text{Re}\{\bar{Z}\} = R$  RESISTANCE (IN OHMS)

defn  $\text{Im}\{\bar{Z}\} = X$  REACTANCE (IN OHMS)

$\bar{Z} = R + jX$  WHERE  $R \in \{\text{REAL NUMBERS}\}$

$X \in \{\text{REAL NUMBERS}\}$



FOR A CAPACITOR  $\bar{Z}_C = \frac{1}{j\omega C}$   $R_C = 0$ ,  $X_C = -\frac{1}{\omega C}$

$$\bar{Z}_C = 0 + j\left(-\frac{1}{\omega C}\right) = \frac{j}{j} \cdot j \cdot \frac{-1}{\omega C} = \frac{(-1)(-1)}{j\omega C} = \frac{1}{j\omega C}$$

FOR AN INDUCTOR  $\bar{Z}_L = j\omega L$   $R_L = 0$   $X_L = \omega L$

$$\bar{Z}_L = 0 + j(\omega L)$$

SIMILARLY FOR ADMITANCE,  $\bar{Y} = \frac{1}{\bar{Z}}$

defn

$\text{Re}\{\bar{Y}\} = G$  CONDUCTANCE (IN SIEMENS)

$\text{Im}\{\bar{Y}\} = B$  SUSCEPTANCE (IN SIEMENS)

$$\bar{Y} = G + jB$$

FOR A CAPACITOR  $\bar{Y} = j\omega C$   $G = 0$ ,  $B = \omega C$

FOR AN INDUCTOR  $\bar{Y} = \frac{1}{j\omega L}$   $G = 0$ ,  $B = -\frac{1}{\omega L}$

$\bar{Y} = \frac{1}{\bar{Z}}$  BUT  $G \neq \frac{1}{R}$  ( $G = \frac{1}{R}$  ONLY IF  $X = 0$ )

AND  $B \neq \frac{1}{X}$

WE HAVE  $\bar{Y} = \frac{1}{\bar{Z}}$

$$G + jB = \frac{1}{R + jX}$$

$$G + jB = \frac{1}{R + jX} \cdot \frac{R - jX}{R - jX} = \frac{R - jX}{R^2 + X^2}$$

$$\therefore G = \frac{R}{R^2 + X^2} \quad B = \frac{-X}{R^2 + X^2}$$

DEFN OF CONDUCTANCE IN PHASOR DOMAIN

WE SAY AN IMPEDANCE IS PURELY RESISTIVE IF  $X = 0$  (A RESISTOR)  
 " " REACTIVE IF  $R = 0$  (INDUCTOR OR CAPACITOR)  
 ADMITANCE " CONDUCTIVE IF  $B = 0$  (CONDUCTOR)  
 " " SUSCEPTIVE IF  $G = 0$  (CAPACITOR OR INDUCTOR)